

## Understanding Logical Effort

Using ngspice, designing a minimum sized CMOS inverter such that the rise time and fall time are equal for a load capacitance of 0.1pF.

(We shall use the time taken to traverse from 10% to 90% of the transient as the rise/fall delay).

The n channel transistor W is  $0.6\mu\text{m}$  and L is  $0.4\mu\text{m}$ . Channel length of p channel transistor should also be  $0.4\mu\text{m}$ . Adjust the width of the p channel transistor to get equal rise and fall times.

For this process, we shall take  $V_{DD}$  to be 3.3V.

CMOS inverter such that the rise time and fall time are equal for a load capacitance of 0.1pF.

Let  $\lambda=90\text{n}$ ,

$L_{\min} = 2\lambda$

Source Area = Drain area =  $W \times 4\lambda = 2 \times W \times L_{\min}$ .

Source Perim. = Drain Perim. =  $2(W + 4\lambda) = 2(W + 2L_{\min})$


The n channel transistor W is  $0.6\mu\text{m}$  and L is  $0.4\mu\text{m}$ . Channel length of p channel transistor is also  $0.4\mu\text{m}$ . Adjusting the width of the p channel transistor to get equal rise and fall times.

Width turns out to be  $1.55795\mu\text{m}$ .


After measurements for transient analysis, rise time turned out to be 1.063718 nsec and fall time was 1.063717 nsec. Where time taken to traverse from 10% to 90% of the transient is considered as the rise/fall delay.

Also, the Inverter delay measured between 50% positions i.e. 1.65V on the transients at the input and output is .5774116 nsec.


Minimum size Inverter with 0.1pf load.

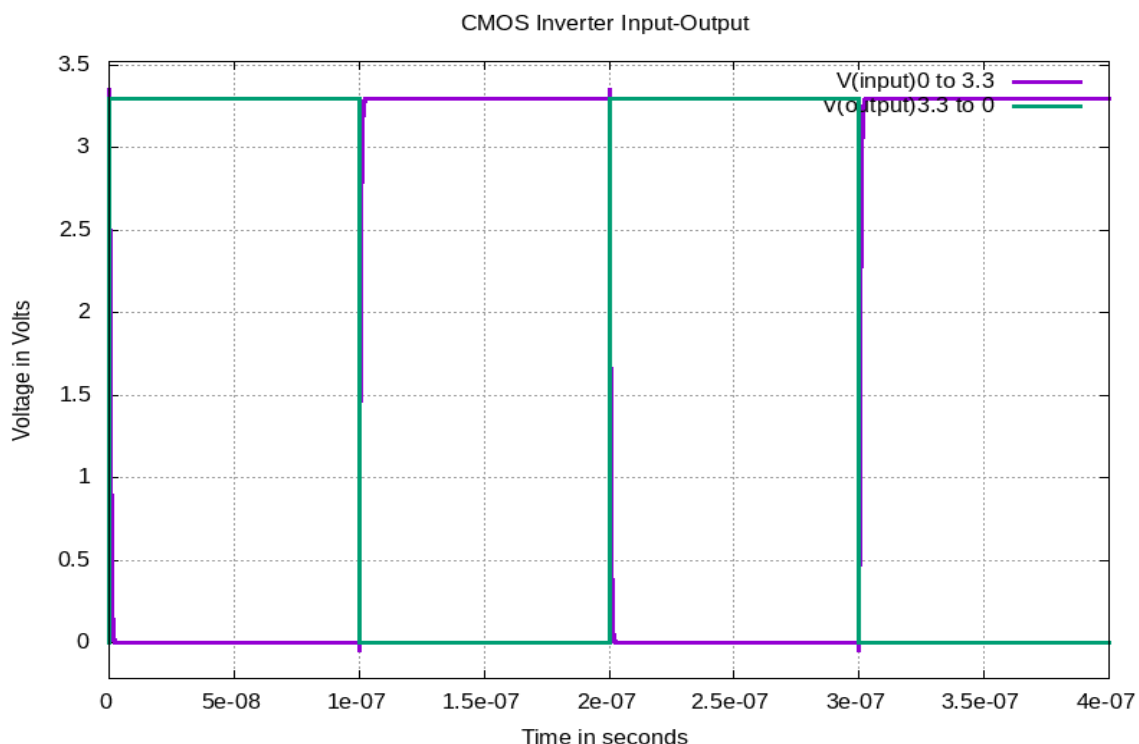

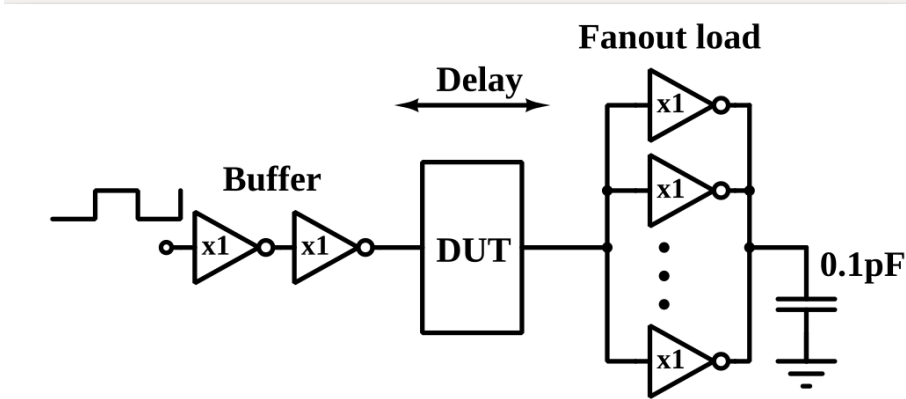Loading the DUT with 1, 2, 3, . . . 8 inverters.





DUT input output waveform

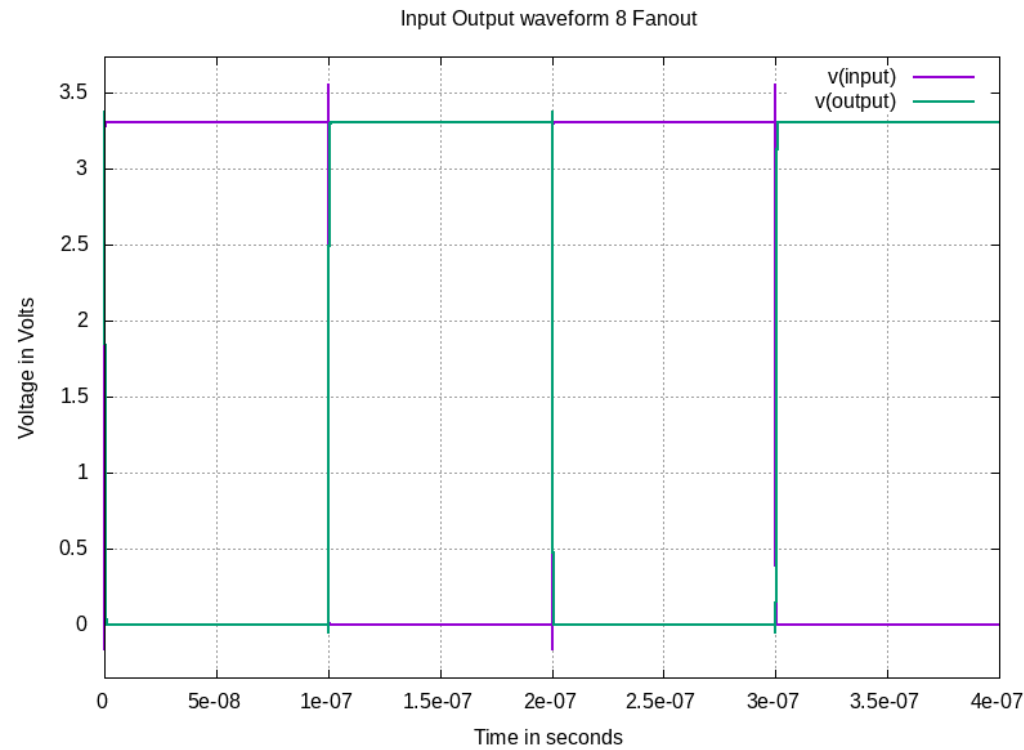


## Observations:

Measurements for Transient Analysis 1 Fanout Load inverter (in seconds)	
Rise time for output capacitor	= 1.066423e-09
Fall time for output capacitor	= 1.067839e-09
Rise time for DUT output	= 7.692229e-11
Fall time for DUT output	= 7.361886e-11
Delay by DUT	= 6.495596e-11
Measurements for Transient Analysis 2 Fanout Load inverter (in seconds)	
Rise time for output capacitor	= 5.527538e-10
Fall time for output capacitor	= 5.540146e-10
Rise time for DUT output	= 1.141917e-10
Fall time for DUT output	= 1.116567e-10
Delay by DUT	= 8.658926e-11
Measurements for Transient Analysis 3 Fanout Load inverter	
Rise time for output capacitor	= 3.898961e-10
Fall time for output capacitor	= 3.909244e-10
Rise time for DUT output	= 1.557521e-10
Fall time for DUT output	= 1.532822e-10
Delay by DUT	= 1.070717e-10
Measurements for Transient Analysis 4 Fanout Load inverter	
Rise time for output capacitor	= 3.167560e-10
Fall time for output capacitor	= 3.173368e-10
Rise time for DUT output	= 2.039521e-10
Fall time for DUT output	= 2.009512e-10
Delay by DUT	= 1.272295e-10
Measurements for Transient Analysis 5 Fanout Load inverter	
Rise time for output capacitor	= 2.796501e-10
Fall time for output capacitor	= 2.797147e-10
Rise time for DUT output	= 2.643911e-10
Fall time for DUT output	= 2.584323e-10
Delay by DUT	= 1.474070e-10
Measurements for Transient Analysis 6 Fanout Load inverter	
Rise time for output capacitor	= 2.602525e-10
Fall time for output capacitor	= 2.595680e-10
Rise time for DUT output	= 3.534234e-10
Fall time for DUT output	= 3.311610e-10
Delay by DUT	= 1.677488e-10
Measurements for Transient Analysis 7 Fanout Load inverter	
Rise time for output capacitor	= 2.499899e-10
Fall time for output capacitor	= 2.484970e-10
Rise time for DUT output	= 4.344415e-10
Fall time for DUT output	= 4.126067e-10
Delay by DUT	= 1.883176e-10
Measurements for Transient Analysis 8 Fanout Load inverter	
Rise time for output capacitor	= 2.459695e-10
Fall time for output capacitor	= 2.438730e-10
Rise time for DUT output	= 4.830160e-10
Fall time for DUT output	= 4.686080e-10
Delay by DUT	= 2.090897e-10

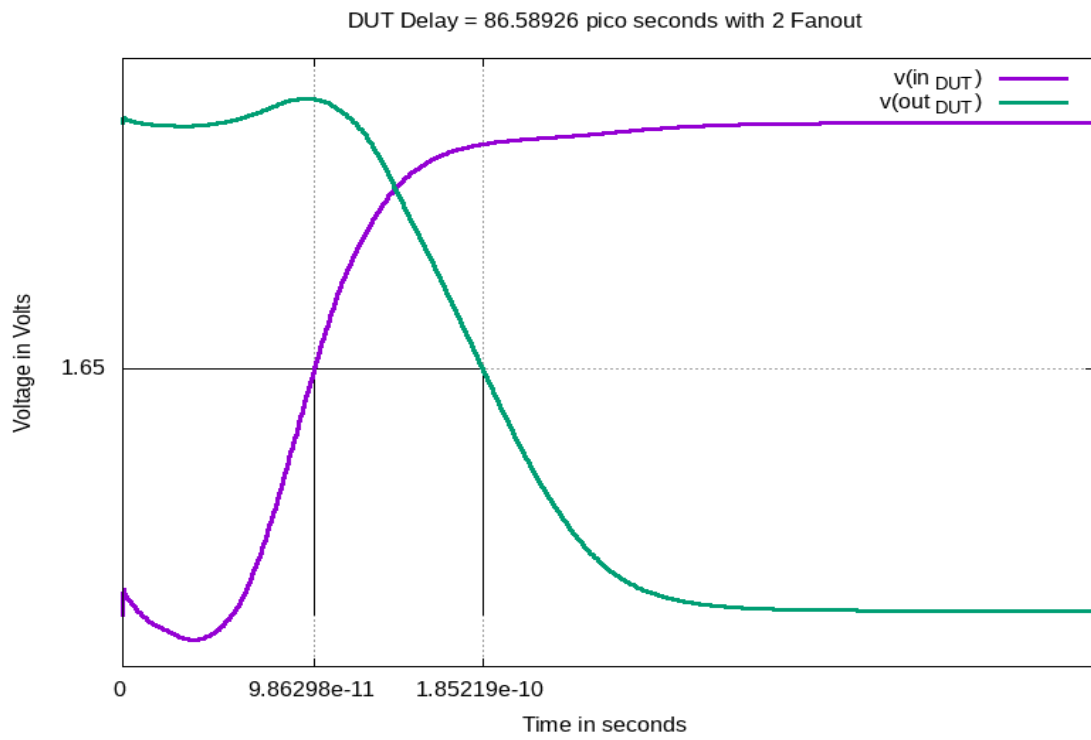 
## Input-Output Delay Characteristicis of DUT



 
DUT Delay = 107.0717 pico seconds with 3 Fanout



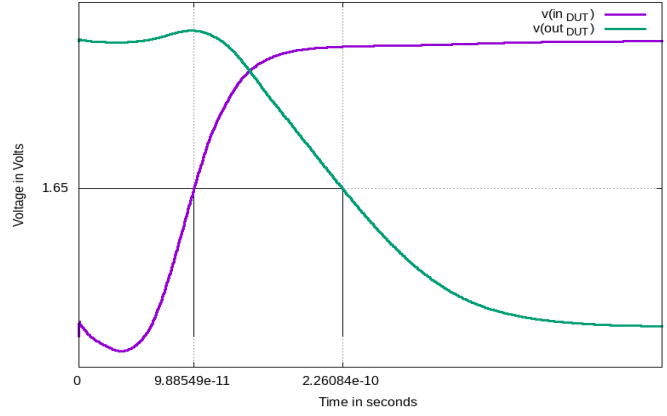
DUT Delay = 127.2295 pico seconds with 4 Fanout



 
DUT Delay = 147.4070 pico seconds with 5 Fanout



 
DUT Delay = 167.7488 pico seconds with 6 Fanout



 DUT Delay = 188.3176 pico seconds with 7 Fanout




 DUT Delay = 209.0897 pico seconds with 8 Fanout



Plotting Fanout vs Delay of DUT,

FANOUT	Delay (in pico seconds)
1	64.95596
2	86.58926
3	107.0717
4	127.2295
5	147.407
6	167.7488
7	188.3176
8	209.0897

 

Evaluating  $\tau$  and  $p_{inv}$

From graph

$$p_{inv}\tau = 4.51697607142857 \times 10^{-11}$$

where,

$$\tau = 2.04736509523811 \times 10^{-11}$$

So,

$$p_{inv} = 4.51697607142857 \times 10^{-11} / 2.04736509523811 \times 10^{-11}$$

$$p_{inv} = 2.216872509103$$